

# 1204 - Digital Systems Design Lab

(Spring 2020)

## Tutorial 2 Circuits


**Pantelis I. Kaplanoglou**

Department of Information and Electronic Engineering

International Hellenic University




# NOT

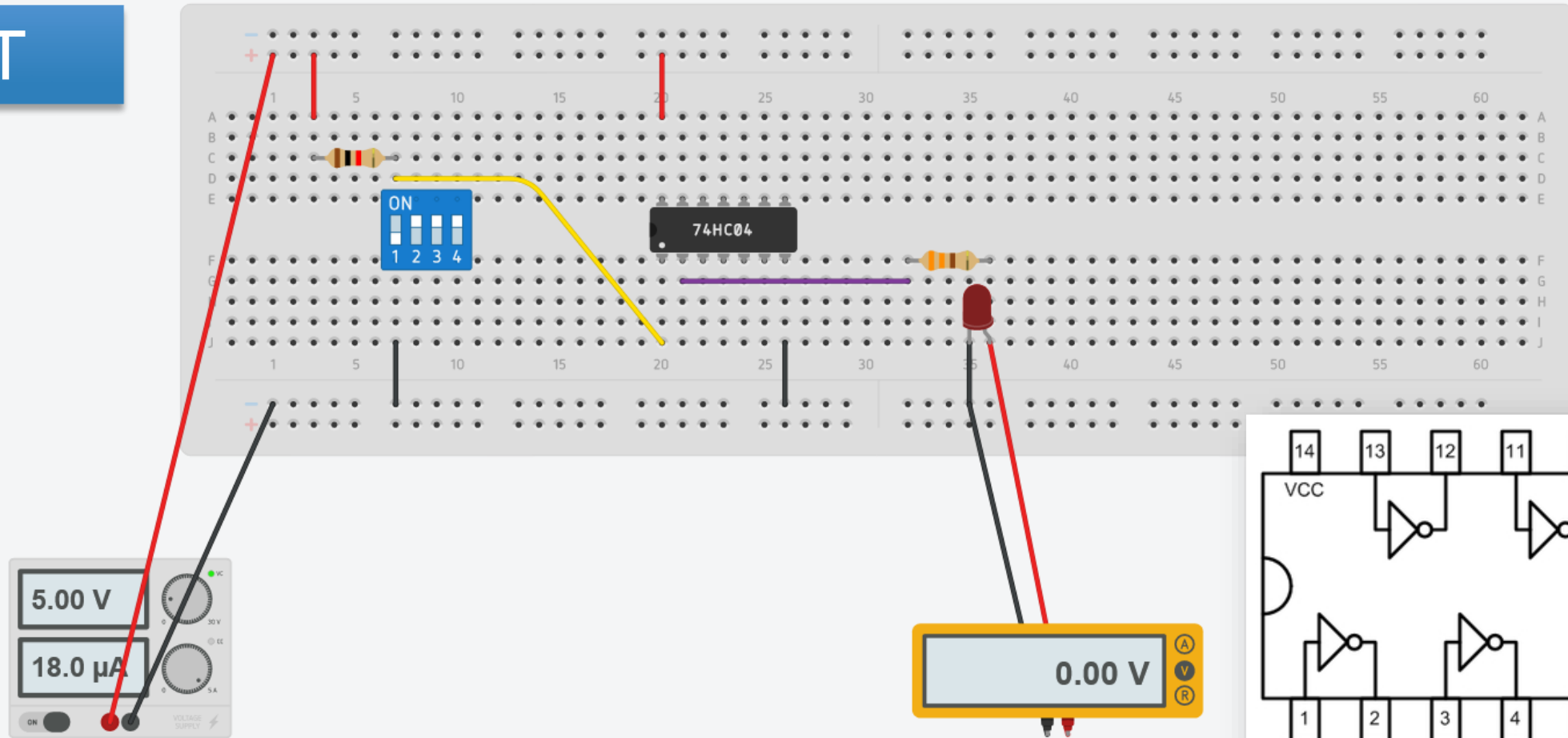

- ▶ This circuit implements NOT using **74HC04**.
- ▶ Switch 1 is at OFF position to signal digit “1” on the yellow wire. The yellow wire is the input of the 1<sup>st</sup> NOT gate in the DIP.
- ▶ The purple wire is the output from the 1<sup>st</sup> NOT gate.




# AND

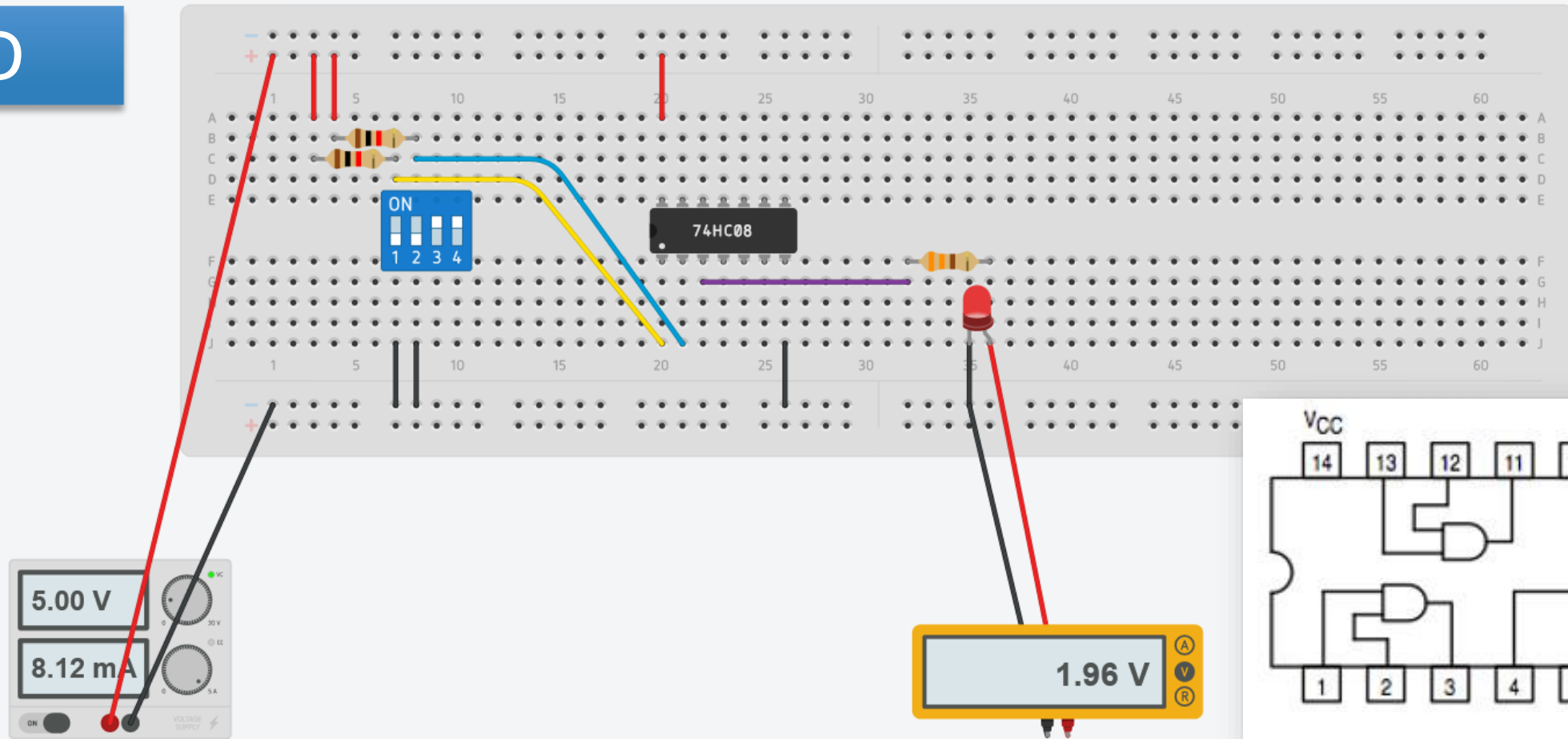

- ▶ This circuit implements AND using **74HC08**.
- ▶ Switches 1 and 2 are both OFF to signal “1” on the yellow and “1” on the blue wire. These are inputs of the 1<sup>st</sup> AND gate in the DIP.
- ▶ The purple wire is the output from the 1<sup>st</sup> AND gate.




# OR

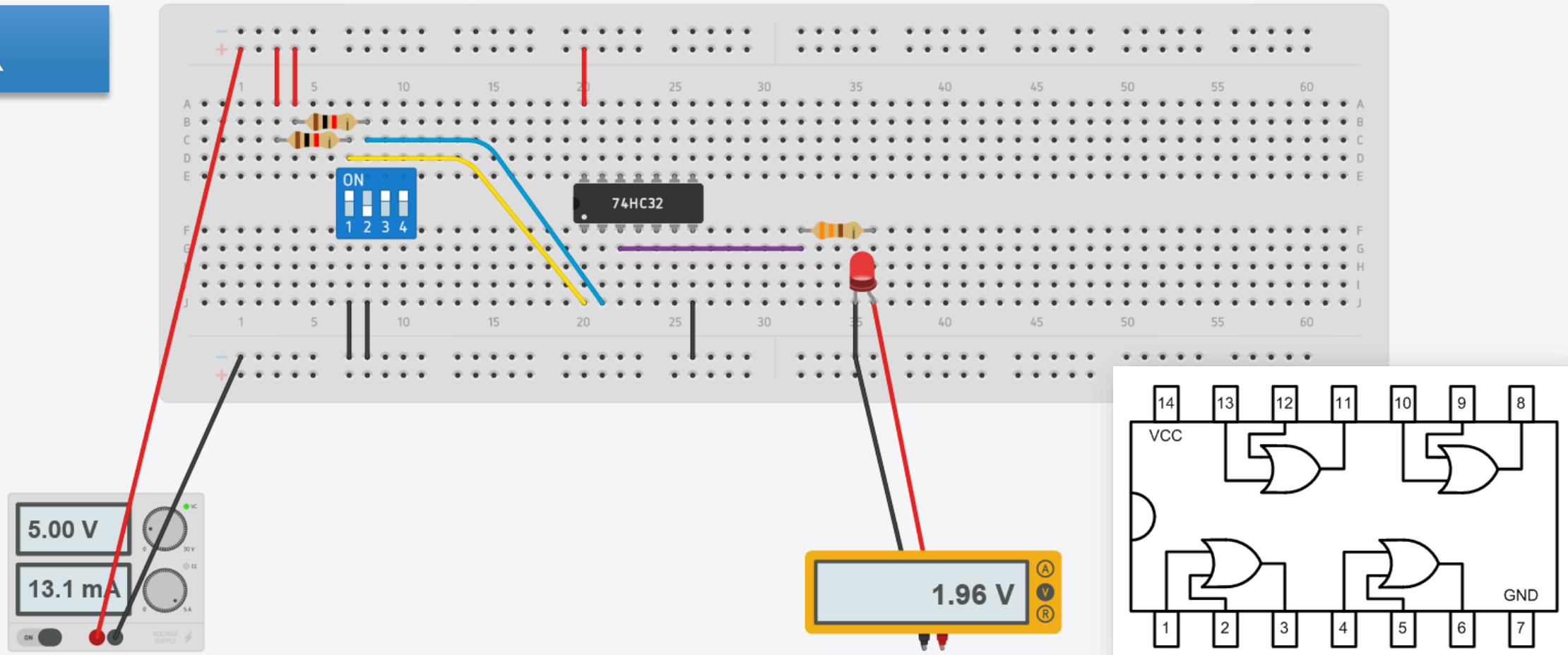

- ▶ This circuit implements OR using **74HC32**.
- ▶ Switch 2 is OFF to signal “1” on the blue wire. Yellow and blue are inputs of the 1<sup>st</sup> OR gate in the DIP.
- ▶ The purple wire is the output from the 1<sup>st</sup> OR gate.




# NOR

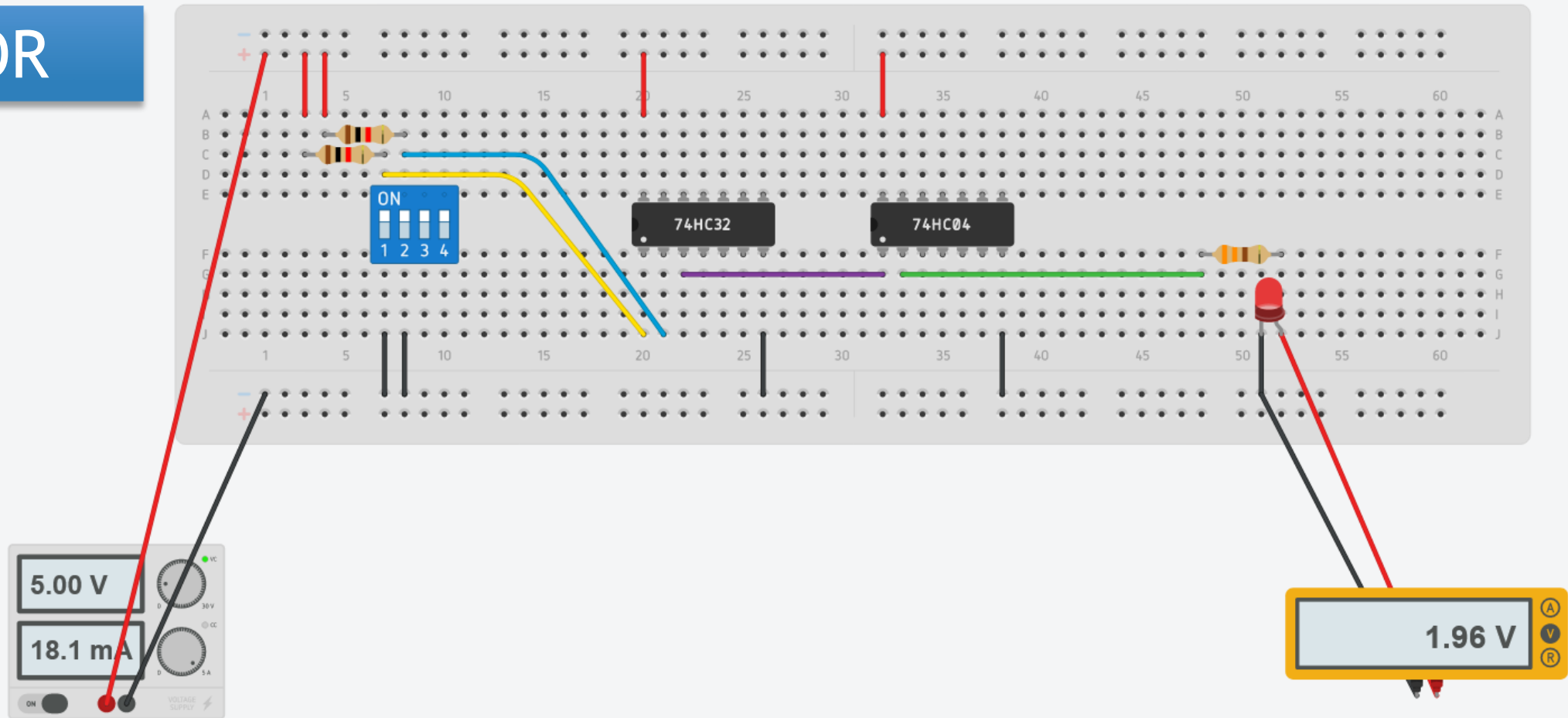

- ▶ This circuit implements NOR using **74HC32** and **74HC04**.
- ▶ Switches are both ON to signal “0” on the blue and “0” on the yellow wire. These are inputs of the 1<sup>st</sup> OR gate in the DIP.
- ▶ The green wire is the inverted output of the 1<sup>st</sup> OR gate.



# NAND

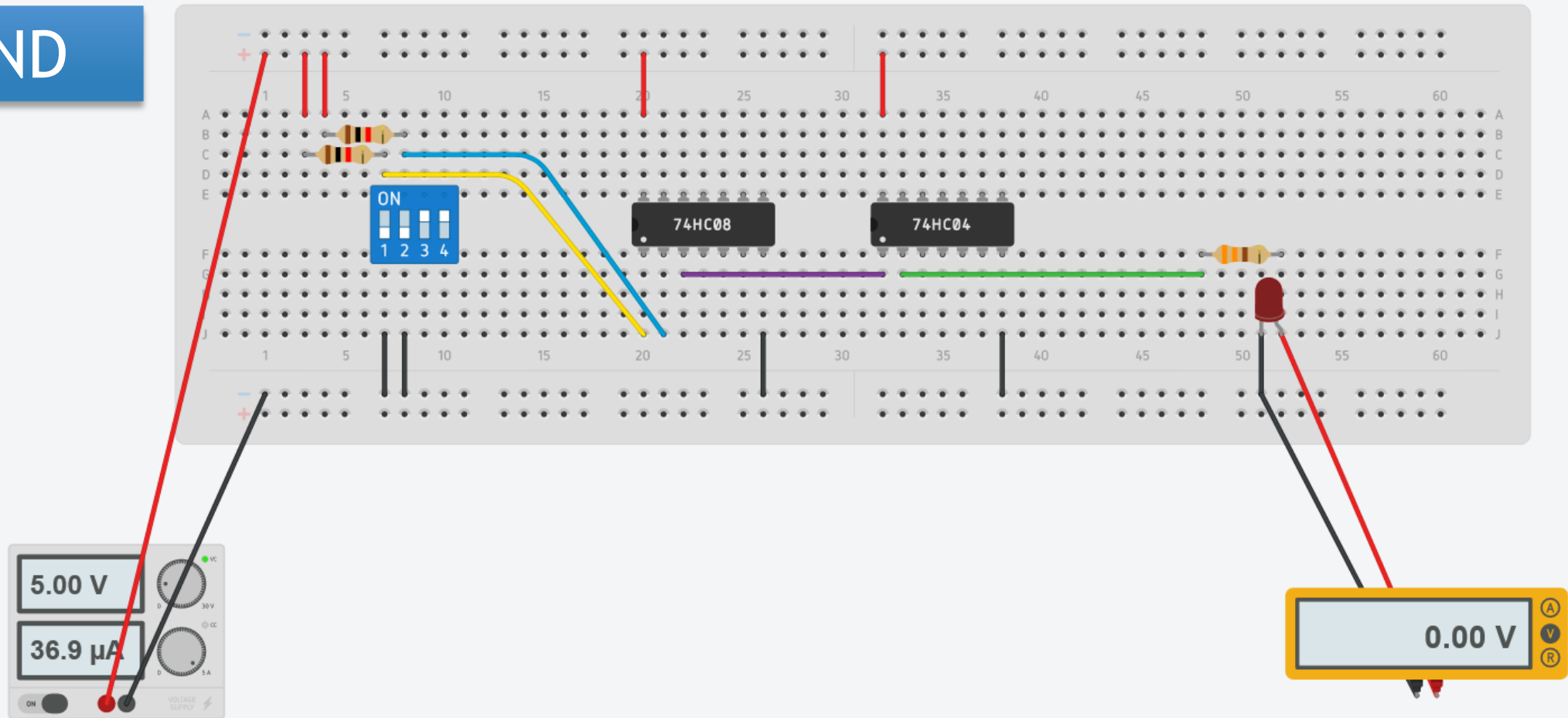


- ▶ This circuit implements NAND using **74HC08** and **74HC04**.
- ▶ Switches are both OFF to signal “1” on the blue and “1” on the yellow wire. These are inputs of the 1<sup>st</sup> AND gate in the DIP.
- ▶ The green wire is the inverted output of the 1<sup>st</sup> AND gate.





# XOR

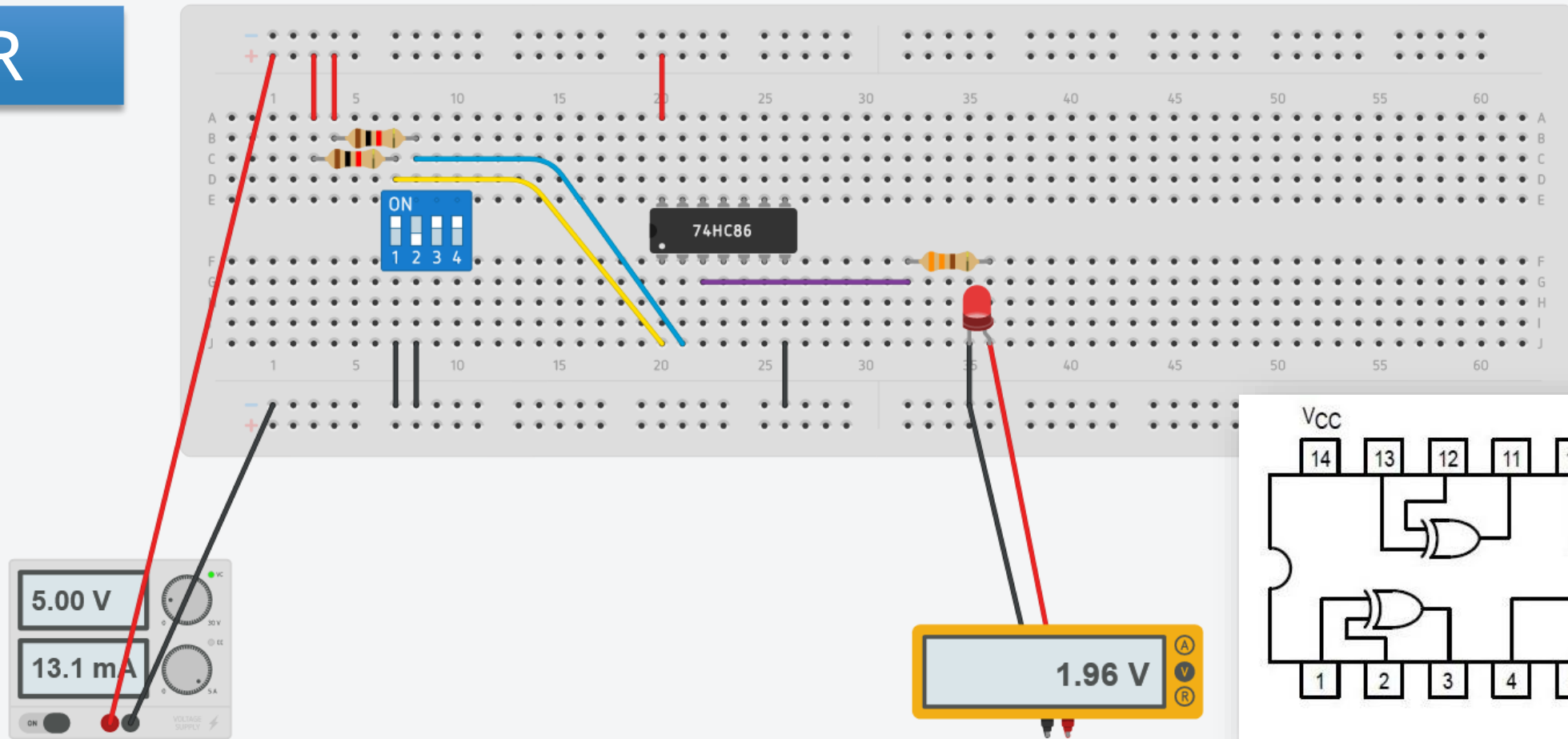

- ▶ This circuit implements XOR using **74HC86**.
- ▶ Switch 2 is OFF to signal “1” on the blue wire. Yellow and blue are inputs of the 1<sup>st</sup> XOR gate in the DIP.
- ▶ The purple wire is the output from the 1<sup>st</sup> XOR gate.

